 


This project will serve to set the standard for project development this semester. Please perform the project and document according to this description.


### **DESCRIPTION**

Using the techniques taught in class regarding HDL design create a register file that has 32 registers 32-bits wide (32 x 32). The register file will have a synchronous write port and two asynchronous read ports. On the active edge of the clock, if write=1, then the 16 bits on WriteData will be written into the register referenced by WriteAddress.  $\text{REG}[\text{WriteAddress}] \leftarrow \text{WriteData}$ . The contents of the register referenced by each ReadAddress will immediately be presented on the read data port.  $\text{ReadData} \leftarrow \text{REG}[\text{ReadAddress}]$ .

### **BLOCK DIAGRAM**



### Test Bench

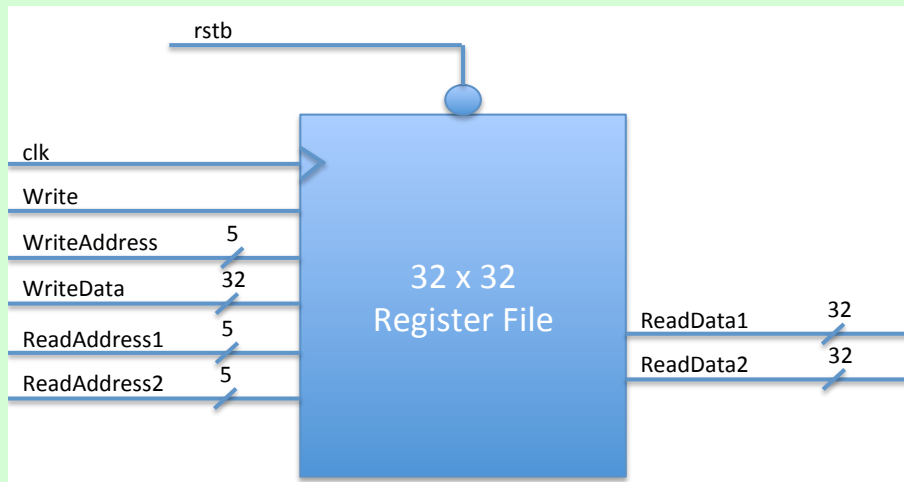

### VERIFICATION

1. Create the design using the Verilog style taught in class
2. Organize your code so that it is intuitive with respect to its functionality
3. Add a header at the beginning to document the design - name, data, purpose
4. Create a test bench using the same module name with “\_tb”
5. Verify the design using simulation
6. Write a report describing the assignment and your work
7. Include a description of the verification
8. Include your source code with the report
9. Demonstrate to instructor
10. Hand in report and upload it to BeachBoard dropbox